



HACETTEPE UNIVERSITY  
COMPUTER ENGINEERING DEPARTMENT

BM233 LOGIC DESIGN LAB - 2020 FALL

---

## Experiment 5 - Sequential Circuits in Verilog

---

December 26, 2020

*Student name*  
İlayda ATMACA

*Student Number:*  
b21827101

## 1 Include the problem statement.

In this experiment, we aim to designing and simulating sequential circuits in Verilog HDL. A flip flop is a basic building block of sequential logic circuits. We have 2 D Flip Flops in the experiment and each of D Flip Flops has two input(x,y), a clock input, reset input and outputs Q and Q' (the inverse of Q). Additionally, we use the sequential circuit so outputs depend on both the present inputs and the sequence of past inputs.

## 2 Convert the given state transition diagram to state transition table.

present	state	input		next	state	output	
A	B	x	y	A	B	F1	F2
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	0	1
0	1	0	0	1	0	1	0
0	1	1	0	1	0	1	0
0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	0	0
1	0	1	0	1	0	1	0
1	0	1	1	1	1	1	1
1	1	0	0	0	0	0	0
1	1	0	1	0	0	0	0
1	1	1	0	1	0	1	0
1	1	1	1	1	1	1	1

Figure 1: State transition table

- 3 Determine the number of D flip flops you need to use to store the state information, and derive the input and output equations from the state transition table. Minimize the functions using K-Maps

 


Figure 2: K-Map

 


Figure 3: K-Map

- 4 Use the simplified functions to obtain the design schematic that uses D flip flops.

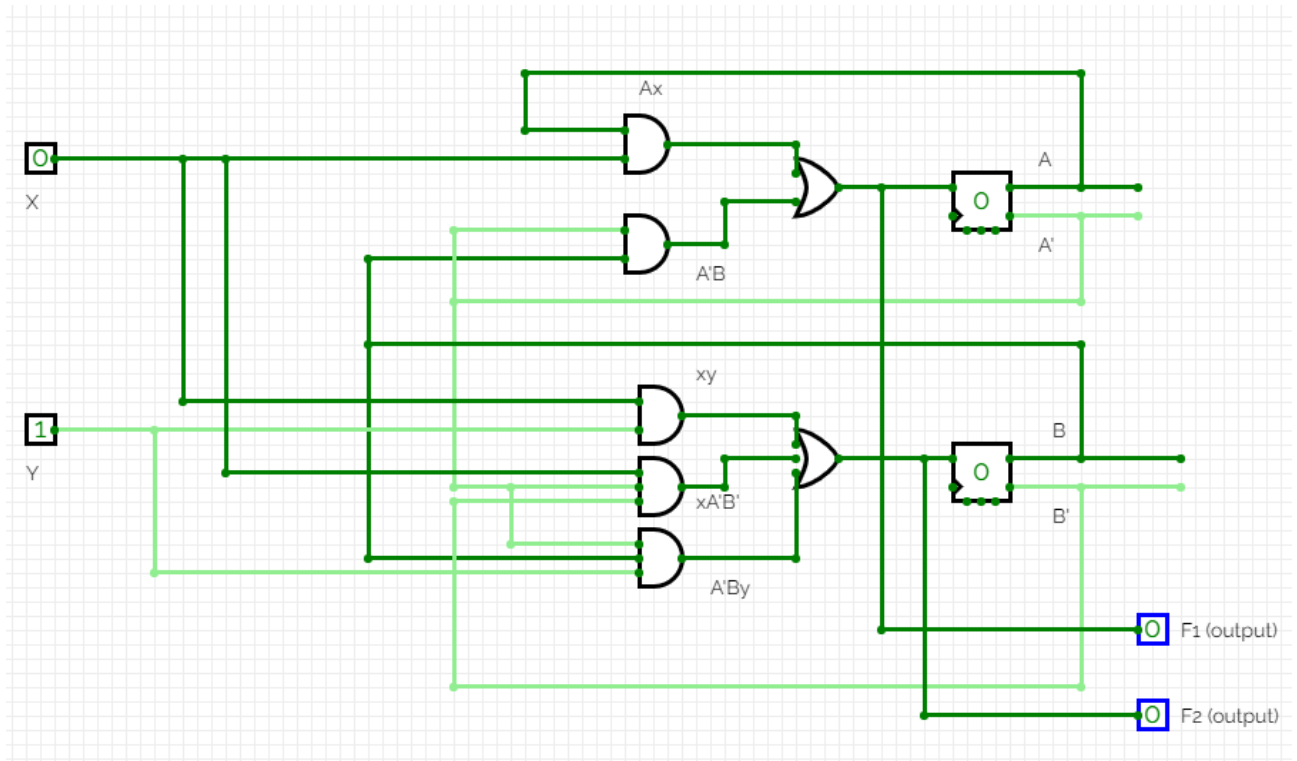


Figure 4:

**5 Include three Verilog code solutions for all specified modules:  
Dflipflop.v, controller.v, and controller<sub>t</sub>b.v**

```

1
2  `timescale 1ns / 1ps
3
4  module Dflipflop(D,clock,reset,Q);
5      input D,clock,reset; //data ,clock,reset input
6      output reg Q;      //output Q
7
8      always @(posedge clock) begin
9          if(reset)
10             Q<=0;
11          else
12             Q<=D;
13          end
14  endmodule

```

```

1
2
3  `timescale 1ns / 1ps
4
5  module controller(input x,
6  input y,input clock,
7  input reset,
8  output [1:0] out
9  );
10
11  reg [1:0] present_state = 2'b00;
12  wire [1:0] next_state;
13  wire w1,w2,w3,w4,w5;
14
15
16  and A1(w1,~present_state[1],present_state[0]);
17  and A2(w2,present_state[1],x);
18  and A3(w3,x,~present_state[0],~present_state[1]);
19  and A5(w5,y,x);
20  and A4(w4,y,~present_state[1],present_state[0]);
21  or o1(out[1],w1,w2);
22  or o2(out[0],w3,w4,w5);
23
24  //Instantiate two D flip flops
25  Dflipflop df(.D((present_state[0]&~present_state[1])|(present_state[1]&x)),
26  .clock(clock),.reset(reset),
27  .Q(next_state[1]));
28
29  Dflipflop df1(.D((~present_state[0]&~present_state[1]&x)

```

```

30 |(present_state[0]&~present_state[1]&y)|(y&x)),
31 .clock(clock),.reset(reset),
32 .Q(next_state[0]));
33
34 always @(reset or next_state)begin
35     if(reset) begin present_state <= 2'b00; end
36     else begin present_state <= next_state; end
37     end
38
39 endmodule

1
2
3
4 `timescale 1ns / 1ps
5 module controller_tb;
6
7 reg x;    //input x,y,clock,reset
8 reg y;
9 reg clock;
10 reg reset;
11 wire [1:0] out; //output out
12
13 controller c(.x(x),.y(y),.clock(clock),.reset(reset),.out(out));
14 initial begin
15     clock = 0;
16     reset = 1;
17     #100;
18     reset = 0;
19     #100;
20     end
21 //Generate a clock with period
22     always #10 clock = ~clock;
23 initial begin //Test sequence
24     x=0; y=0;
25     #100 x=0; y=0;
26     #100 x=1; y=0;
27     #100 x=0; y=0;
28     #100 x=0; y=1;
29     #100 x=1; y=1;
30     #100 x=1; y=0;
31     #100 x=1; y=1;
32     #100 x=0; y=1;
33     end
34 endmodule

```

## 6 Include the obtained waveform.

 


Figure 5: Waveform

 


Figure 6: Waveform

## 7 Explain the obtained results and how they show that your design is working correctly.

First, I created my truth table and K-map from my state diagram. and I obtained the boolean equations from the K-map. I also got information on how output depends on the inputs. The outputs can change when clock edge will be either rising edge or falling edge. and when I compared my truth table and vaweform, I saw that I got the correct values.

## References

- Reference 1: [https://en.wikipedia.org/wiki/Flip-flop\\_\(electronics\)#](https://en.wikipedia.org/wiki/Flip-flop_(electronics)#)
- Reference 2: [https://www.electronics-tutorials.ws/sequential/seq\\_4.html#](https://www.electronics-tutorials.ws/sequential/seq_4.html#)